



ИСПИТ ИЗ ОСНОВА ЕЛЕКТРОТЕХНИКЕ 1

19. 10. 2015. - Рјешења

1.

$$R_2 = 22,5 \text{ cm.}$$

2.

а)

$$E = \frac{q}{\varepsilon_0 (\varepsilon_{r1} + \varepsilon_{r2}) r \pi}, \quad a \leq r \leq b.$$

$$D_1 = \frac{\varepsilon_{r1} q}{(\varepsilon_{r1} + \varepsilon_{r2}) r \pi}, \quad a \leq r \leq b,$$

$$D_2 = \frac{\varepsilon_{r2} q}{(\varepsilon_{r1} + \varepsilon_{r2}) r \pi}, \quad a \leq r \leq b.$$

б) $\varepsilon_{r2} = 3.$

в) $C = 667 \text{ pF.}$

г) $E_{\max} = 10 \frac{\text{MV}}{\text{m}}.$

3.

а) $P_{13} = 800 \text{ mW.}$

б) $P_{E4} = 3 \text{ W, (генератор).}$

4.

а) $\Delta Q_1 = -62,5 \mu\text{C},$

$$\Delta Q_2 = 250 \mu\text{C}.$$

б) $P_{E1}^{P2Z} = 187,5 \text{ W.}$

$$P_{E2}^{P1Z} = P_{E2}^{P2Z} = 0,$$