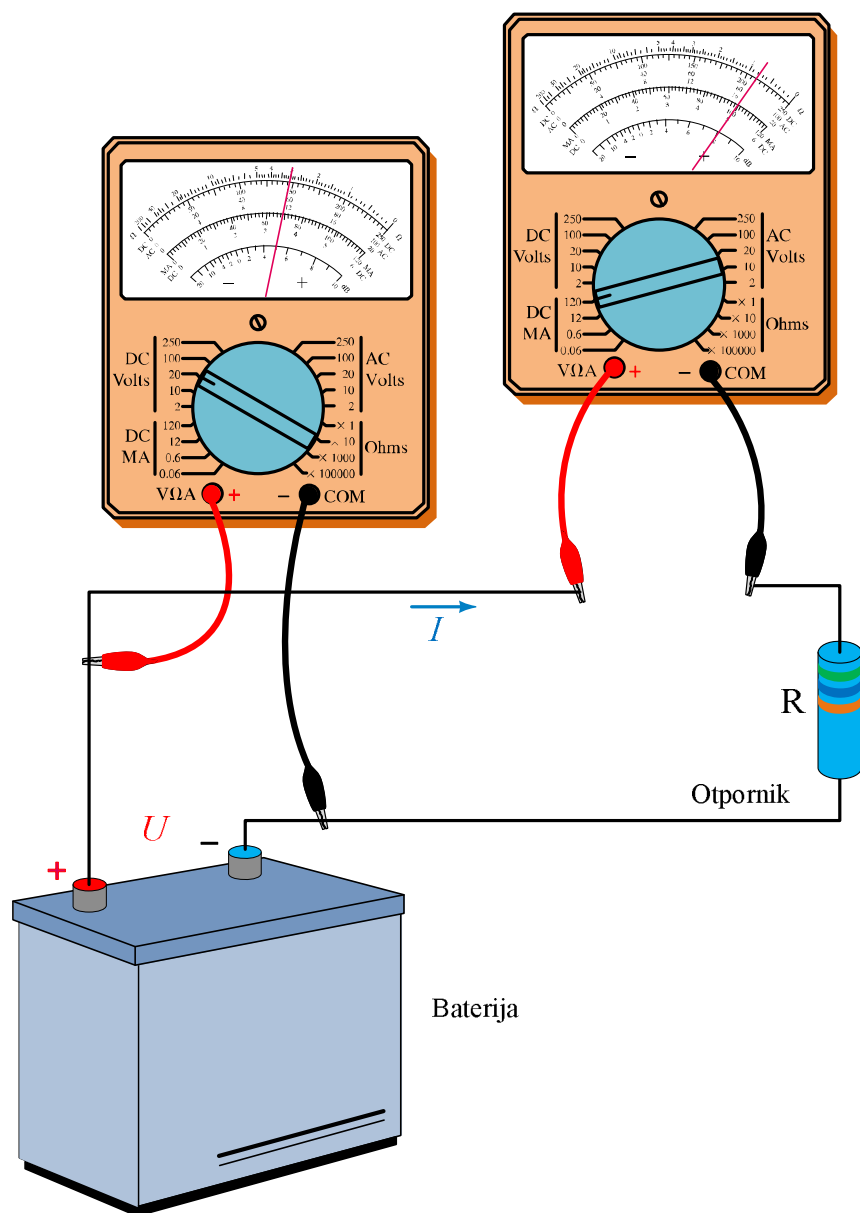


Omov zakon u električnom kolu




Om je eksperimentalno dokazao da je struja u kolu direktno proporcionalna priključenom naponu a obrnuto proporcionalna otpornosti kola







$$I = \frac{U}{R}$$

$$R = \frac{U}{I}$$

$$U = I \cdot R$$

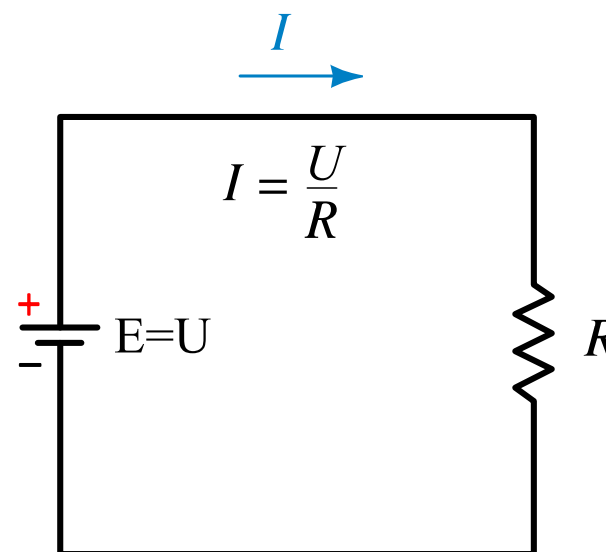

Primjena Ohmovog zakona

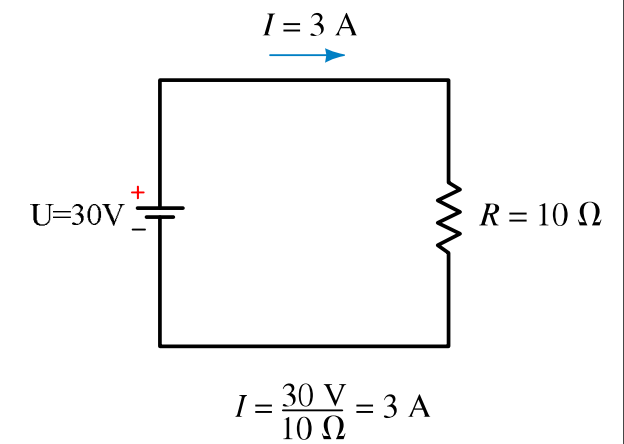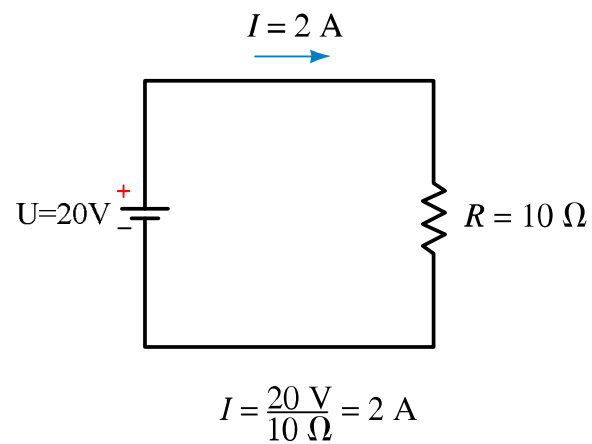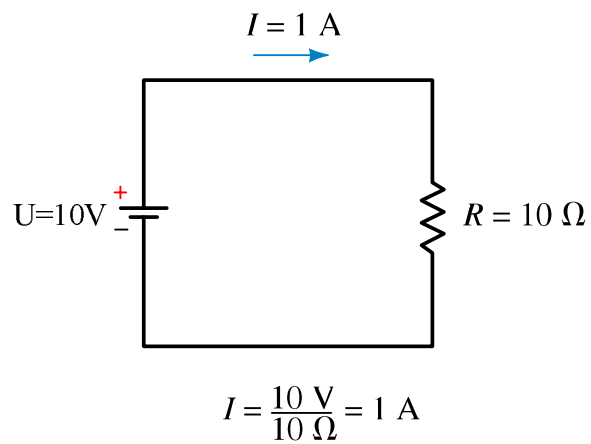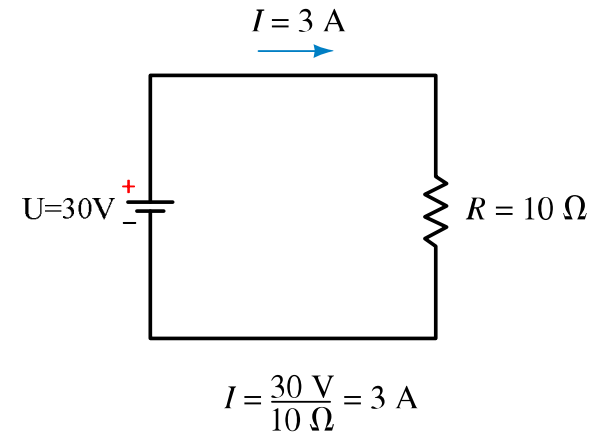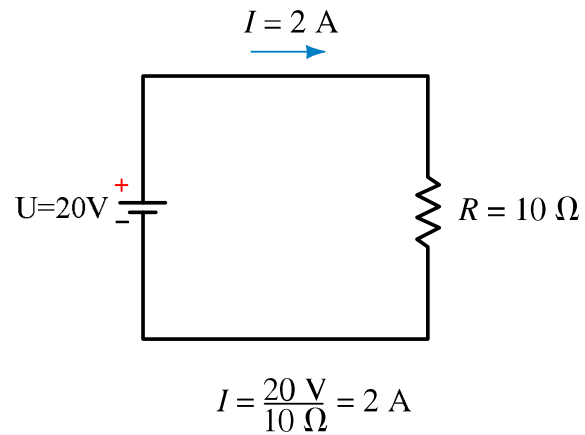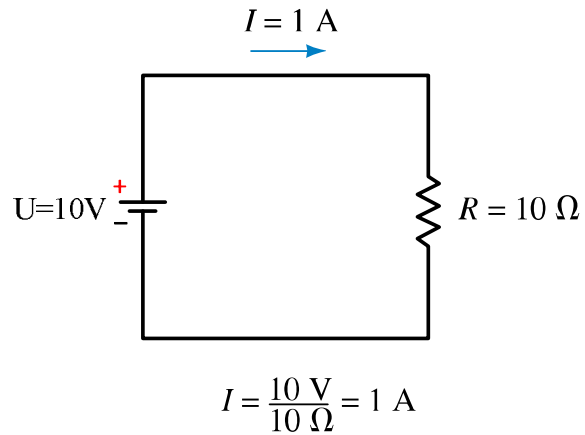

Omov zakon u električnom kolu

Primjer:

 **EXAMPLE 4-1** A $27\text{-}\Omega$ resistor is connected to a 12-V battery. What is the current?

Solution Substituting the resistance and voltage values into Ohm's law yields

$$I = \frac{E}{R} = \frac{12\text{ V}}{27\text{ }\Omega} = 0.444\text{ A}$$

Omov zakon u električnom kolu

Primjer:

EXAMPLE 4-2 The lamp of Figure 4-4 draws 25 mA when connected to a 6-V battery. What is its resistance?

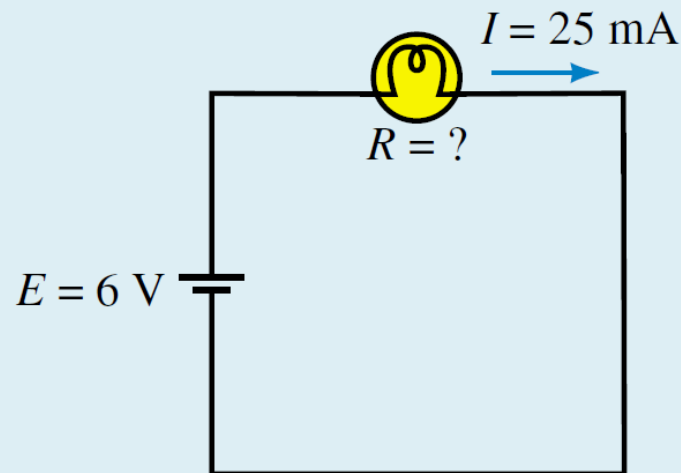



FIGURE 4-4

Solution Using Equation 4-3,


$$R = \frac{E}{I} = \frac{6\text{ V}}{25 \times 10^{-3}\text{ A}} = 240\ \Omega$$

Omov zakon u strujnom kolu (prekid kola i kratki spoj)

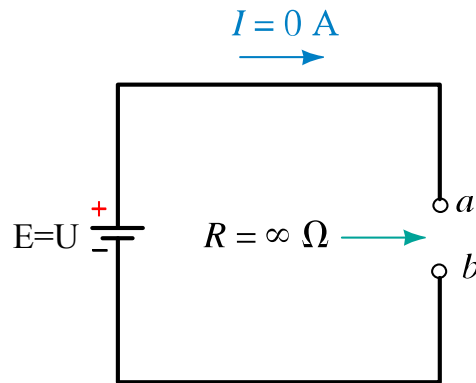- U slučaju **prekida kola** struja kroz kolo ne teče pa je **otpor kola beskonačan**
- U slučaju **kratkog spoja** u kolu vrijednost struja u kolu je teoretski **beskonačna** (u praksi ima veliku vrijednost) a **otpor u kolu je nula** (u praksi ima veoma malu vrijednost)


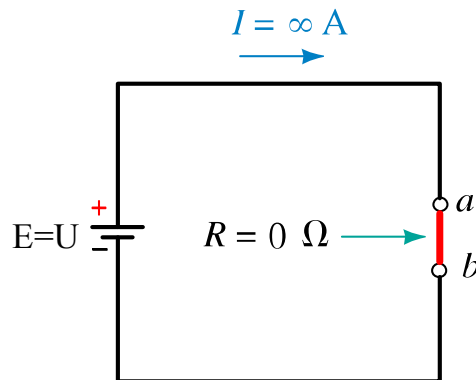
$$I = \frac{U}{R} = \frac{U}{\infty} = 0 A$$




$$I = \frac{U}{R} = \frac{U}{0} = \infty A$$

Omov zakon (pad napona na otporniku)


- U prostom strujnom kolu struja koja protiče na otporniku pravi **pad napona** U_R koji je jednak:

$$U_R = I \cdot R$$

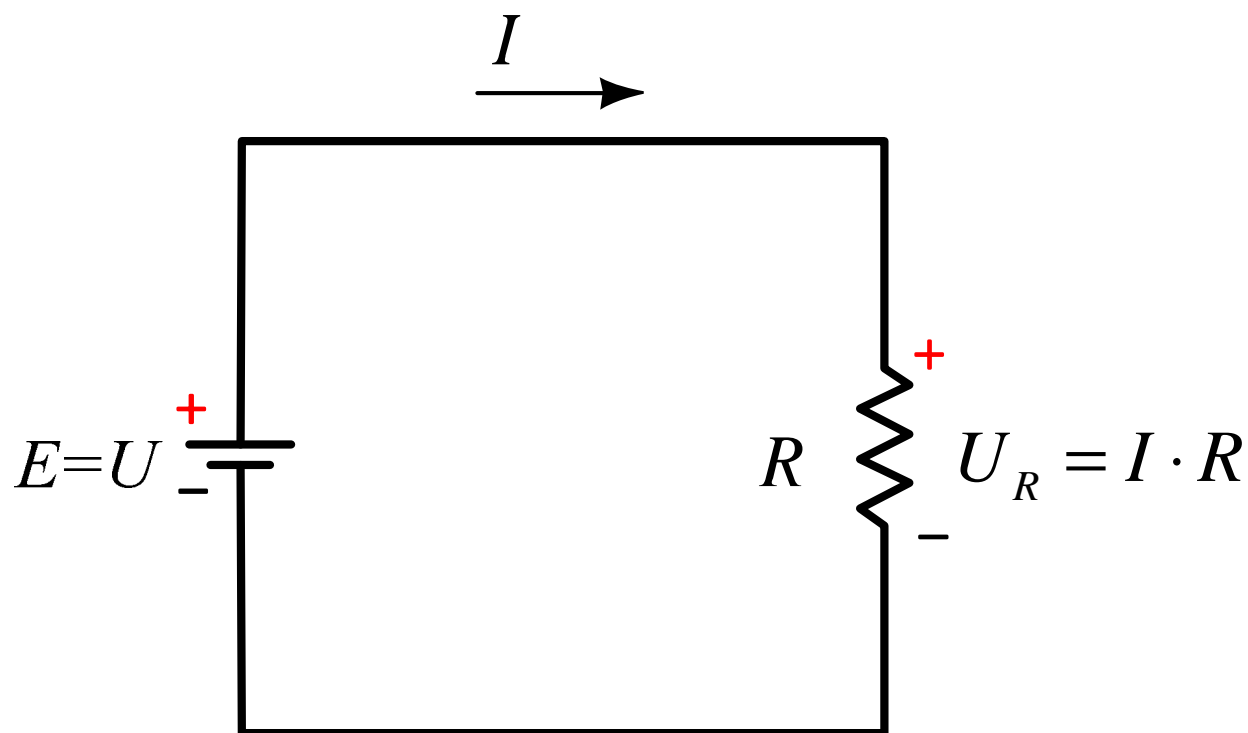

Omov zakon (pad napona na otporniku)

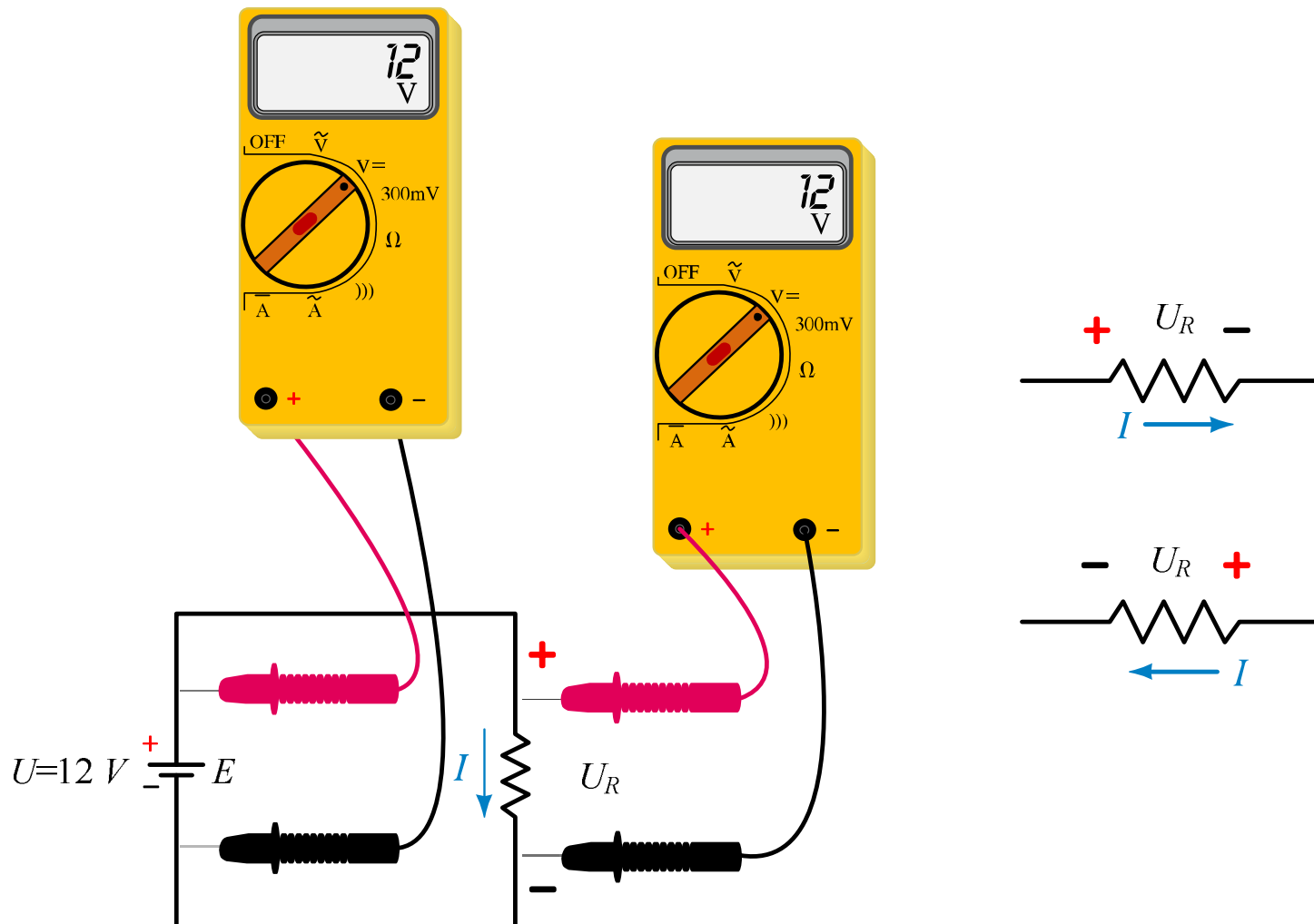- Polaritet napona U_R takav da plus pol (+) odgovara ulasku struje u otpornik a minus pol (-) izlasku struje iz otpornika (-)



Omov zakon (pad napona na otporniku)

Primjer:

EXAMPLE 4–5 The current through each resistor of Figure 4–10 is $I = 0.5$ A. Compute V_1 and V_2 .

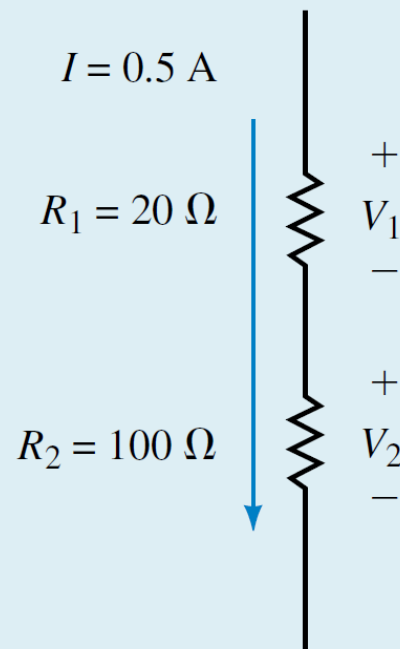



FIGURE 4–10 Ohm's law applies to each resistor.

Solution $V_1 = IR_1 = (0.5\text{ A})(20\ \Omega) = 10\text{ V}$. Note, I is also the current through R_2 . Thus, $V_2 = IR_2 = (0.5\text{ A})(100\ \Omega) = 50\text{ V}$.

Omrov zakon (pad napona na otporniku)


Primjer:

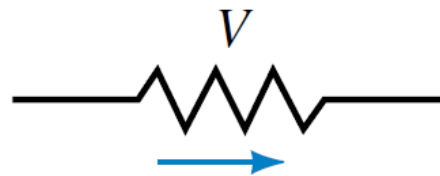For each resistor of Figure 4–12, compute V and show its polarity.




$$I = 0.1 \text{ A}$$

$$(a) R = 10 \text{ k}\Omega$$

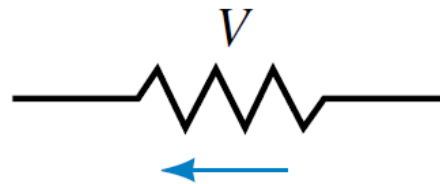


$$I = 0.15 \text{ mA}$$

$$(b) R = 3 \text{ M}\Omega$$

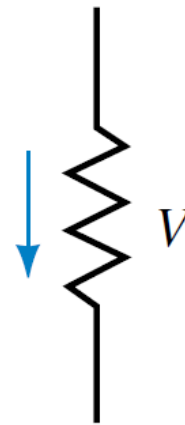

$$I = 0.3 \text{ A}$$

$$(c) R = 400 \Omega$$

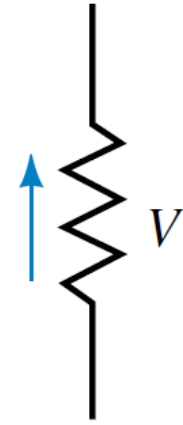

$$I = 2.5 \text{ A}$$

$$(d) R = 0.4 \Omega$$

Pojam električne snage


- Električni uređaji: grijači, sijalice, motori, ... imaju na sebi oznake **60W, 100W, 500W, 1000W**.. Ove oznake predstavljaju **električnu snagu** uređaja
- Intuitivno nam je jano da što je veća snaga uređaja to se više električne energije pretvori u neki drugi oblik : toplotu, svjetlost, mehanički rad itd.
- Tako sijalica od 100W “daje” više svjetlosti od sijalice od 40W
- Motor od 4000W daje više mehaničke snage na osovini od motora od 100W....

Pojam električne snage

- Električna snaga predstavlja brzinu obavljanja rada, odnosno pretvaranja električne energije u neki drugi oblik u nekom posmatranom vremenskom intervalu:

$$P = \frac{A}{t} [W \text{ (} Vat \text{)}]$$

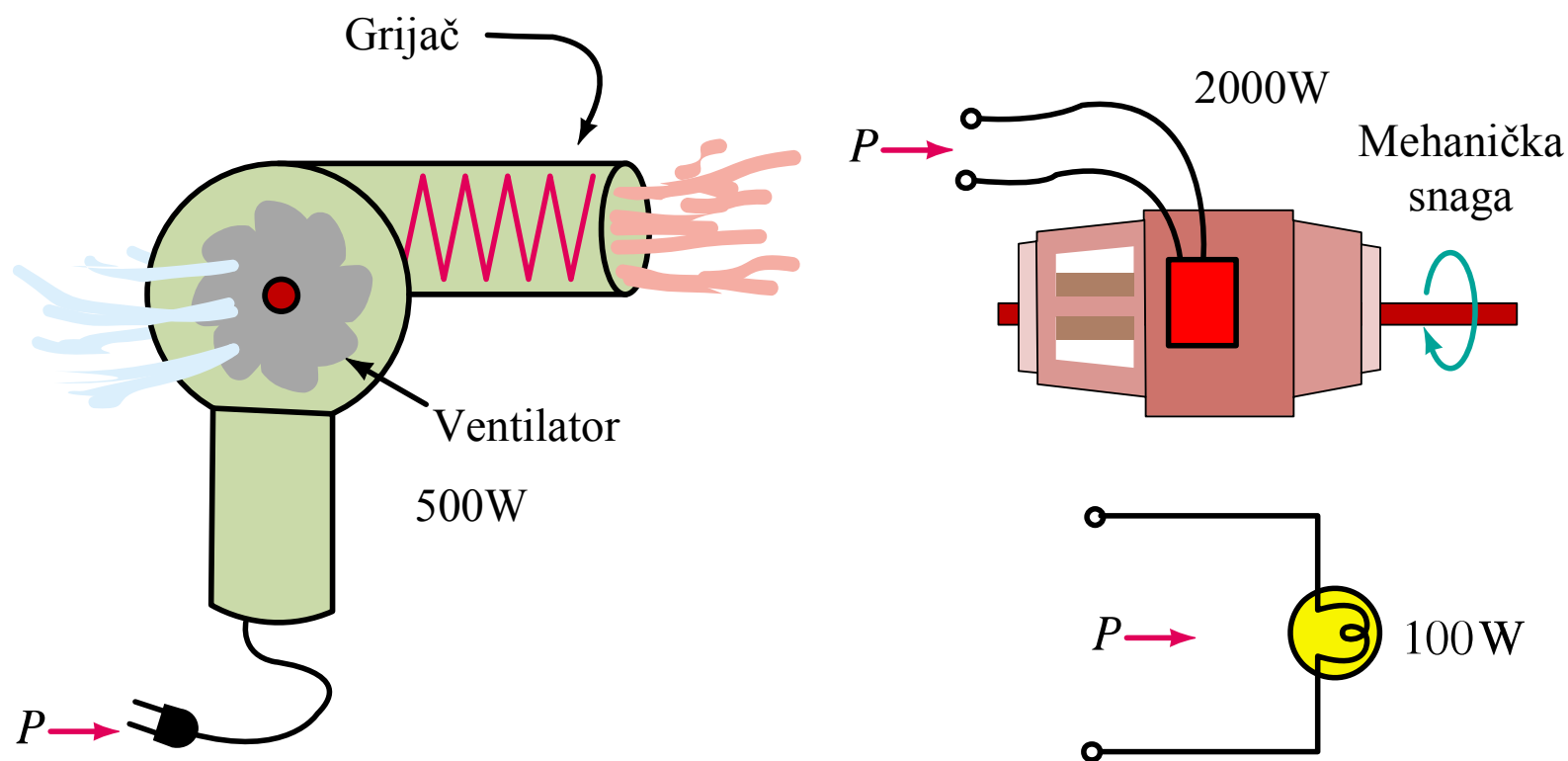- A- Električni rad (energija) – [J (Džul)]
- t – vremenski interval - [s]



Snaga u električkim kolima

- **Podsjetimo se:** Ako se **utrošeni rad** podijeli sa **količinom naelektrisanja** dobije se fizikalna veličina koja se naziva **električni napon** i mjeri se u voltima:

$$U = \frac{A}{Q}$$

- **Podsjetimo se:** Kažemo da je **električna struja** u kolu direktno proporcionalna **količini naelektrisanja** koja protekne u posmatranom **vremenskom intervalu**

$$I = \frac{Q}{t}$$

- Množenjem gornjih jednačina dobijamo izraz za električnu snagu:

$$U \cdot I = \frac{A}{Q} \cdot \frac{Q}{t} = \frac{A}{t} \quad \longrightarrow \quad P = \frac{A}{t} = U \cdot I [1W (Vat)]$$

Snaga u električkim kolima

- U istosmjernim kolima postoji samo **aktivna snaga P** koju izvori troše na **otpornicima**.
- Primjenom Omovog zakona mogu se dobiti ekvivalentni izrazi za električnu snagu:

$$P = U \cdot I, \quad U = I \cdot R$$



$$P = I^2 \cdot R$$

$$P = U \cdot I, \quad I = \frac{U}{R}$$



$$P = \frac{U^2}{R}$$

Snaga u električkim kolima

Primjer:

EXAMPLE 4-6 Compute the power supplied to the electric heater of Figure 4-16 using all three electrical power formulas.

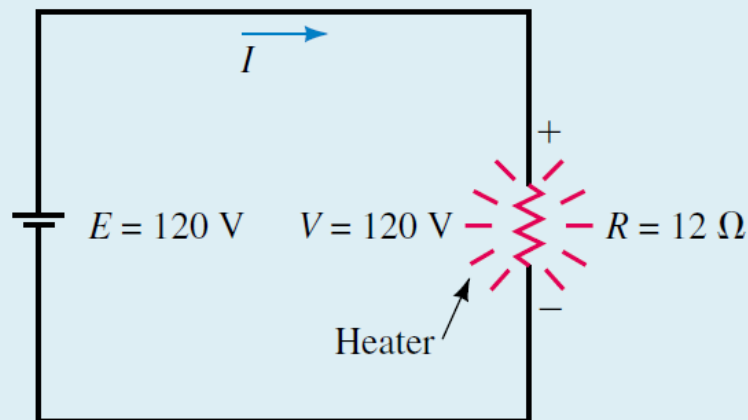


FIGURE 4-16 Power to the load (i.e., the heater) can be computed from any of the power formulas.

Solution $I = V/R = 120\text{ V}/12\ \Omega = 10\text{ A}$. Thus, the power may be calculated as follows:

- a. $P = VI = (120\text{ V})(10\text{ A}) = 1200\text{ W}$
- b. $P = I^2R = (10\text{ A})^2(12\ \Omega) = 1200\text{ W}$
- c. $P = V^2/R = (120\text{ V})^2/12\ \Omega = 1200\text{ W}$

Note that all give the same answer, as they must.

Snaga u električkim kolima

Primjer:

 **EXAMPLE 4–7** Compute the power to each resistor in Figure 4–17 using Equation 4–13.

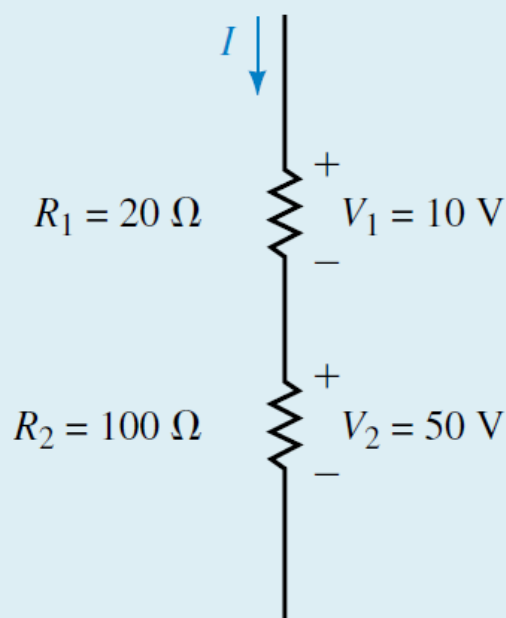



FIGURE 4–17

Solution You must use the appropriate voltage in the power equation. For resistor R_1 , use V_1 ; for resistor R_2 , use V_2 .

a. $P_1 = V_1^2/R_1 = (10\text{ V})^2/20\ \Omega = 5\text{ W}$

b. $P_2 = V_2^2/R_2 = (50\text{ V})^2/100\ \Omega = 25\text{ W}$

Označavanje smijera toka snage u kolu

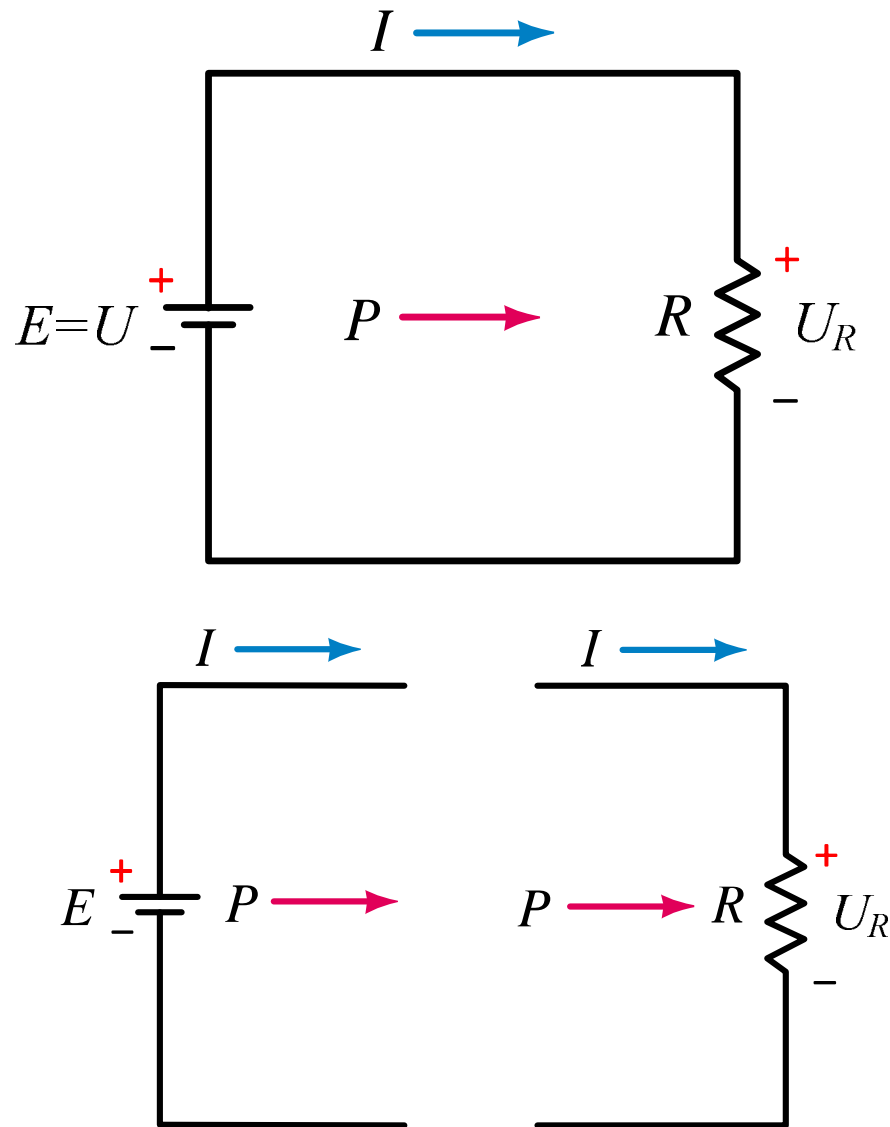

- Za **smijer toka snage** kažemo da je **pozitivan** ako se snaga izvora predaje potrošaču
- Za **snagu izvora** kažemo da je **pozitivna** ako su vrijednosti i napona E i strije I izvora **pozitivne** za usvojene smjerove kao na slici
- Za snagu potrošača kažemo da je pozitivna ako su vrijednosti i napona U_R i strije I potrošača **pozitivne** za usvojene smjerove kao na slici

Pojam električne energije

- Anžagovana snaga u nekom vremenskom intervalu naziva se energija

$$W = P \cdot t \quad [1W \cdot 1s = 1J \text{ (Džul)}]$$

- Ako se vremenski intervali mjere u satima

$$W = P \cdot t \quad [1W \cdot 1h = 1Wh]$$

- Najčešće korišćena jedinica je

$$W = P \cdot t \quad [1kW \cdot 1h = 1kWh]$$

Električna energija

Primjer:

 **EXAMPLE 4–10** Determine the total energy used by a 100-W lamp for 12 hours and a 1.5-kW heater for 45 minutes.

Solution Convert all quantities to the same set of units, e.g., convert 1.5 kW to 1500 W and 45 minutes to 0.75 h. Then,

$$W = (100 \text{ W})(12 \text{ h}) + (1500 \text{ W})(0.75 \text{ h}) = 2325 \text{ Wh} = 2.325 \text{ kWh}$$

Alternatively, convert all power to kilowatts first. Thus,

$$W = (0.1 \text{ kW})(12 \text{ h}) + (1.5 \text{ kW})(0.75 \text{ h}) = 2.325 \text{ kWh}$$

Električna energija

Primjer:

 **EXAMPLE 4–11** Suppose you use the following electrical appliances: a 1.5-kW heater for $7\frac{1}{2}$ hours; a 3.6-kW broiler for 17 minutes; three 100-W lamps for 4 hours; a 900-W toaster for 6 minutes. At \$0.09 per kilowatthour, how much will this cost you?

Solution Convert time in minutes to hours. Thus,

$$\begin{aligned} W &= (1500)(7\frac{1}{2}) + (3600)\left(\frac{17}{60}\right) + (3)(100)(4) + (900)\left(\frac{6}{60}\right) \\ &= 13\,560 \text{ Wh} = 13.56 \text{ kWh} \\ \text{cost} &= (13.56 \text{ kWh})(\$0.09/\text{kWh}) = \$1.22 \end{aligned}$$

Uređaji za mjerenje potrošnje električne energije

- Električno brojilo je uređaj kojim se mjeri i registruje električna energija isporučena potrošaču.
- Za domaćinstva se mjeri i obračunava samo aktivna energija P , a mjerna jedinica je kilovatsat (kWh)
- U zavisnosti o vrsti električnog priključka domaćinstva brojila mogu biti jednofazna ili trofazna. Dvotarifna i višetarifna brojila mogu odvojeno registrovati potrošnju u razdobljima utvrđenih tarifnim sistemom

